

# Digital Circuits and Systems Lab

Laboratory report submitted for the partial fulfillment  
of the requirements for the degree of

*Bachelor of Technology*  
*in*  
*Electronics and Communication Engineering*

by

Nehil Sood 19UEC036

Course Coordinator  
Dr. Kusum Lata



Department of Electronics and Communication Engineering  
The LNM Institute of Information Technology, Jaipur

August 2020

Copyright © The LNMIIT 2020  
All Rights Reserved

## Contents

Chapter	Page
1 Experiment - 1 . . . . .	1
1.1 Aim . . . . .	1
1.2 Theory . . . . .	1
1.2.1 Half Adder . . . . .	1
1.2.2 Full Adder . . . . .	1
1.3 Coding Techniques used . . . . .	1
1.4 Simulation and Results . . . . .	2
1.4.1 Half Adder using Dataflow . . . . .	2
1.4.2 Half Adder using Behavioural . . . . .	3
1.4.3 Full Adder using Dataflow . . . . .	4
1.4.4 Full Adder Using Behavioural modeling . . . . .	5
1.4.5 Full adder Using Structural . . . . .	6
1.5 Summary . . . . .	7

## **Chapter 1**

### **Experiment - 1**

#### **1.1 Aim**

Design, simulate and implement Half adder, Full adder using dataflow, behavioral and structural modeling in VHDL.

#### **1.2 Theory**

##### **1.2.1 Half Adder**

Half Adder adds two binary digits where the input bits are termed as augend and addend and the result will be two outputs one is the sum and the other is carry. To perform the sum operation, XOR is applied to both the inputs, and AND gate is applied to both inputs to produce carry.

##### **1.2.2 Full Adder**

In the full adder circuit, it adds 3 one-bit numbers, where two of the three bits can be referred to as operands and the other is termed as bit carried in. The produced output is 2-bit output and these can be referred to as output carry and sum.

#### **1.3 Coding Techniques used**

Firstly Half Adder was implemented using Dataflow modelling. Dataflow modelling describes the architecture of the entity without describing its components in terms of flow of data from input towards output.

Then Half Adder was implemented using Behavioral modelling. In Behavioral modelling, the behaviour of the entity is expressed using sequentially executed. Further we implemented Full Adder using Dataflow and Behavioural. Lastly we implemented Full Adder using Structural Modelling. In this modelling we used small structures. We used the half adder as a component and implemented full adder using it.

# 1.4 Simulation and Results

## 1.4.1 Half Adder using Dataflow

 


Figure 1.1: Schematic of the Half adder using Dataflow modeling

 


Figure 1.2: Project Summary of the Half adder using Dataflow modeling

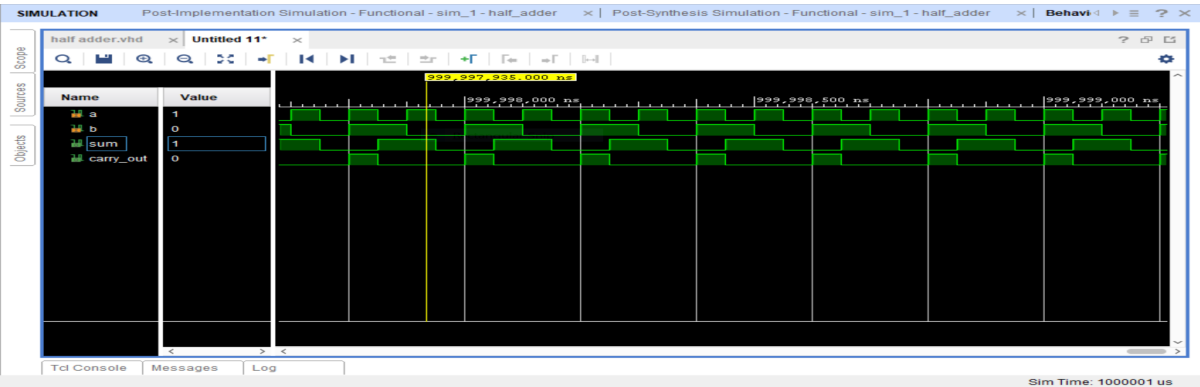


Figure 1.3: Simulation of the Half adder using Dataflow modeling

1.4.2 Half Adder using Behavioural

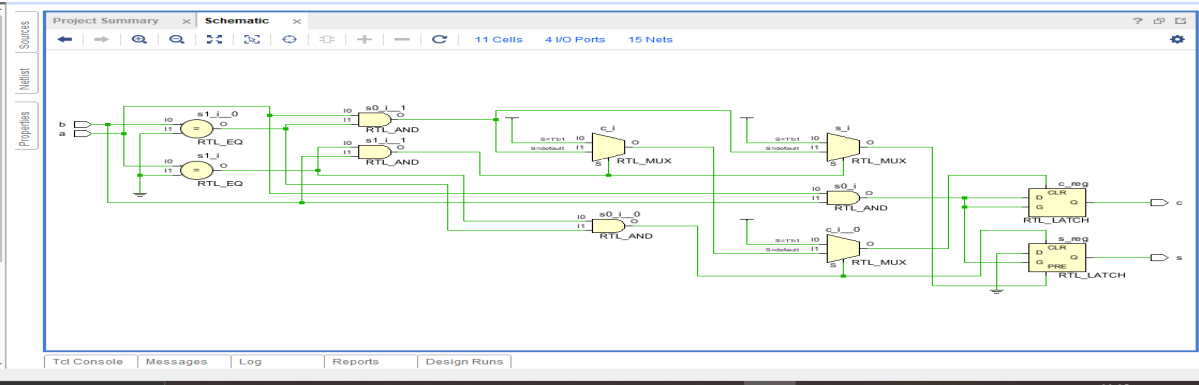


Figure 1.4: Schematic of the Half adder using Behavioural modeling

 


Figure 1.5: Project Summary of the Half adder using Behavioural modeling

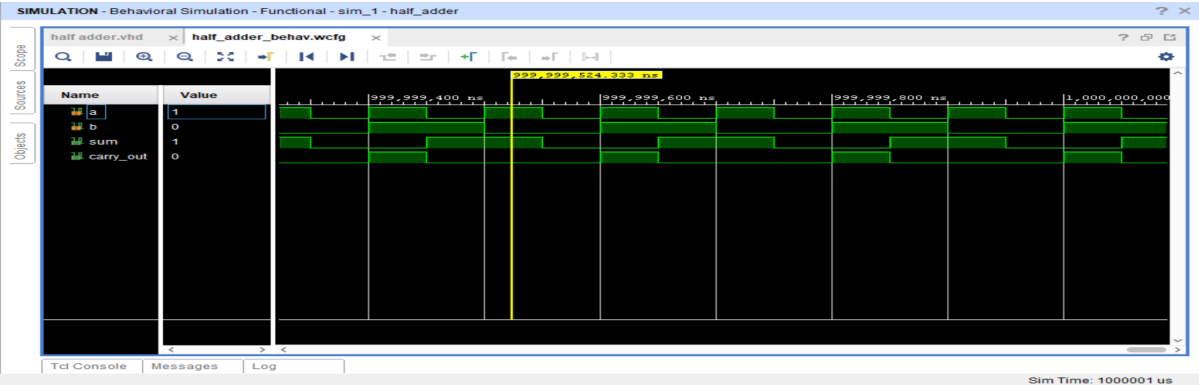


Figure 1.6: Simulation of the Half adder using Behavioural modeling

### 1.4.3 Full Adder using Dataflow

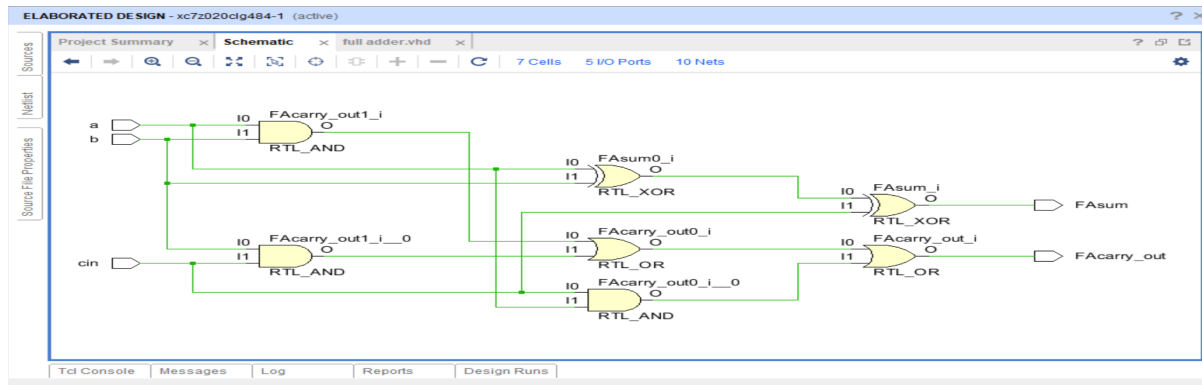


Figure 1.7: Schematic of the Full adder using Dataflow modeling

 


Figure 1.8: Project Summary of the Full adder using Dataflow modeling

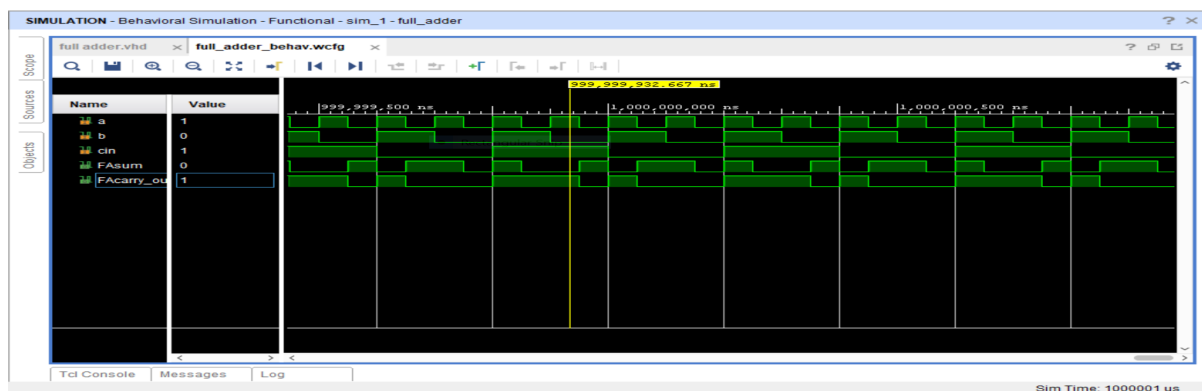


Figure 1.9: Simulation of the Full adder using Dataflow modeling

1.4.4 Full Adder Using Behavioural modeling

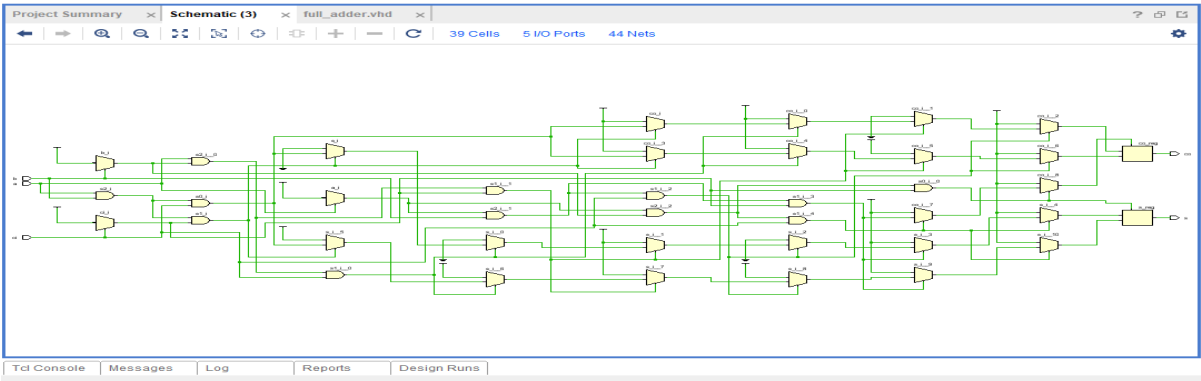


Figure 1.10: Schematic of the Full adder using Behavioural modeling

 


Figure 1.11: Project Summary of the Full adder using Behavioural modeling

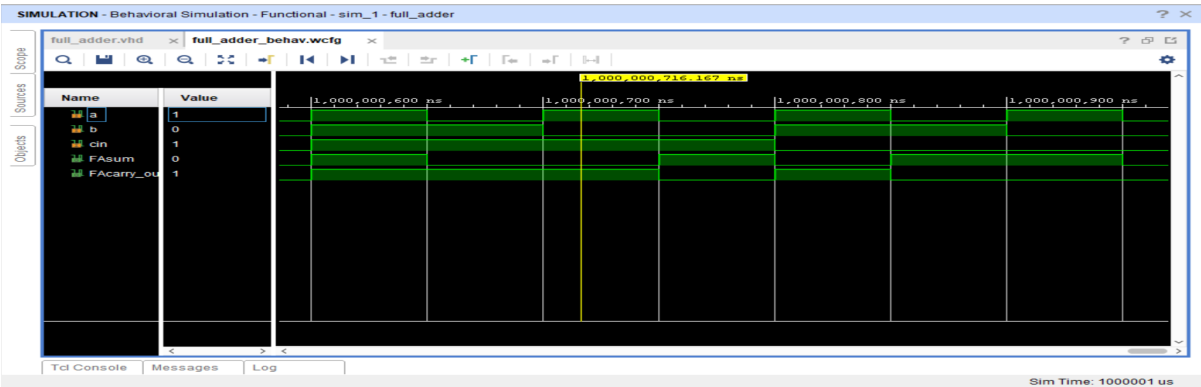


Figure 1.12: Simulation of the Full adder using Behavioural modeling



1.4.5 Full adder Using Structural

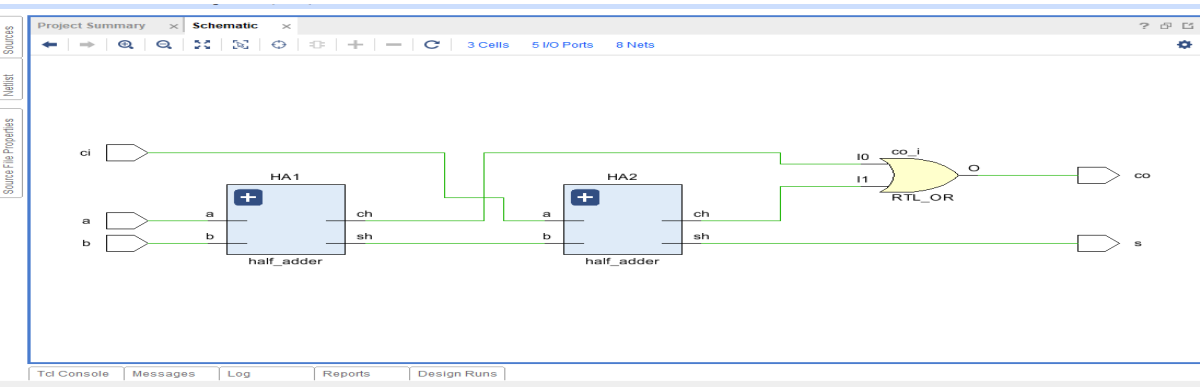


Figure 1.13: Schematic of the Full adder using Structural modeling

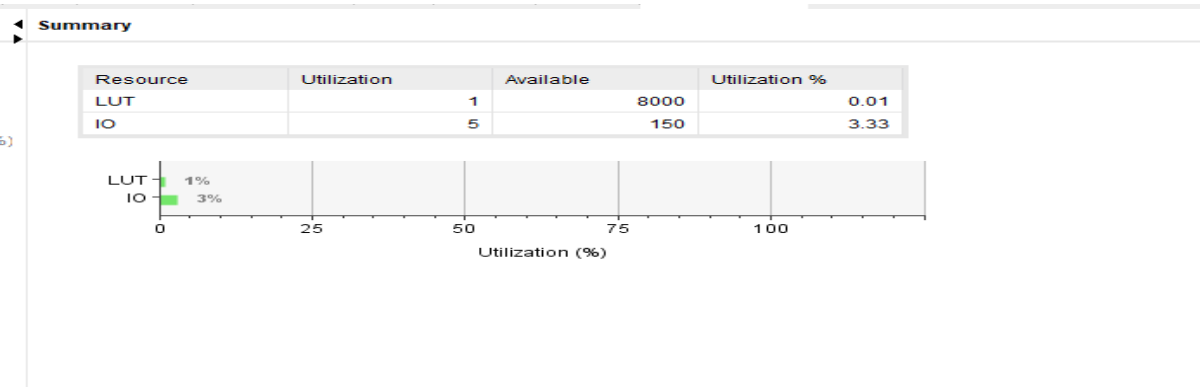


Figure 1.14: Project Summary of the Full adder using Structural modeling

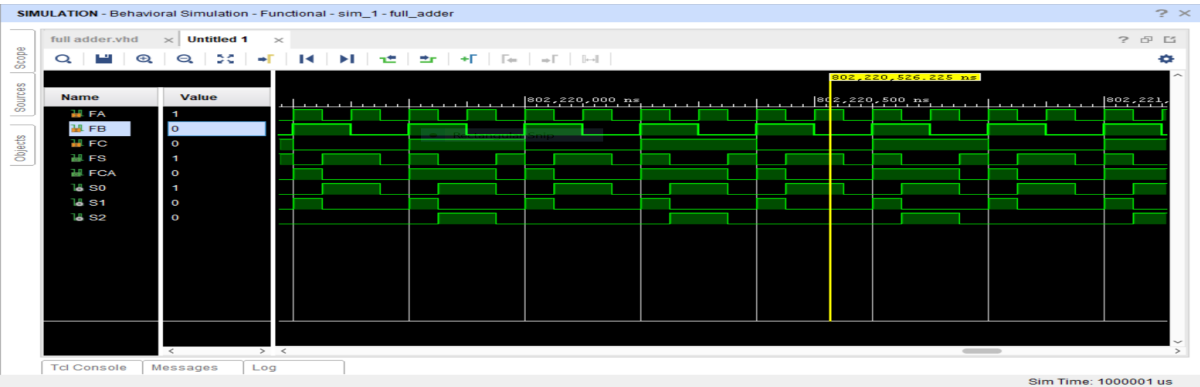


Figure 1.15: Simulation of the Full adder using Structural modeling

## 1.5 Summary

Name of the Entity	No. of LUT used(in percentage)	Total On chip Power(in Watt)
Half Adder using Dataflow	1	0.721
Half Adder using Behavioural	5	0.208
Full Adder using Dataflow	1	0.956
Full Adder using Behavioural	4	0.101
Full Adder using Structural	1	0.957

**Table 1.1** comparison of Area and power requirements for different kinds of adders.